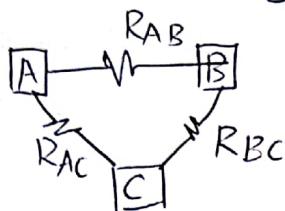


Spring 2018

Problem 5


a) Smart bandage



$R_{AB}, R_{BC}, R_{AC} \rightarrow$ Skin resistances


$50\Omega - 150\Omega$

Wound healed Not healed

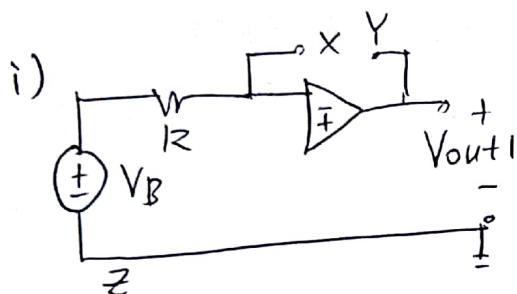

Target: $V_{out1} = \text{function}(R_{AB}, R, V_B)$
 $V_{out1} \neq \text{function}(R_{BC}, R_{AC})$

What if we have the following?

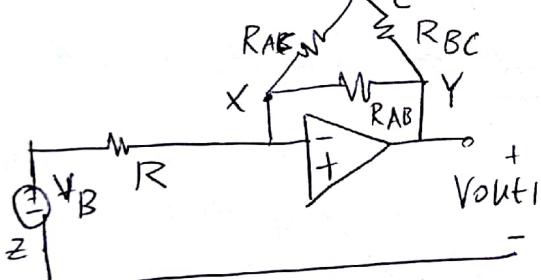

Inverting amplifier

$$V_{out1} = -\frac{R_{eq, XY}}{R} V_B$$


$$= -\frac{R_{AB} || (R_{AC} + R_{BC})}{R} V_B$$

↑ function of R_{AC}, R_{BC}

- Not a valid solution


* Also we need to connect C to any of the three nodes: X, Y, Z.

New approach

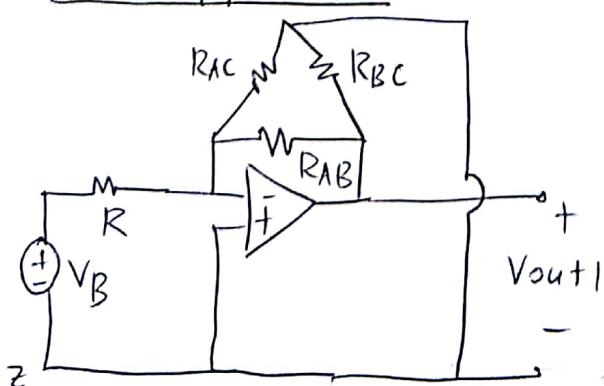

Is V_{out1} a function of $R_{AC} \times R_{BC}$ now?

Clue: Redraw & simplify

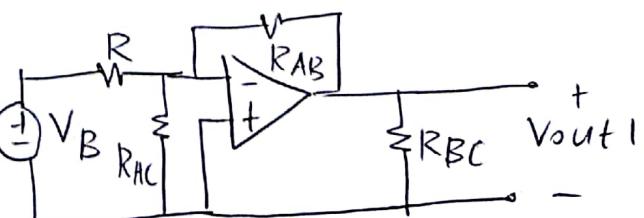

* Is $V_{out1} = f(R_{BC})$?

Op-amp output V_{out1} is not a function of R_{BC}
 $V_{out1} \neq f(R_{BC})$
 (R_{BC} is virtually the load here, which does not change opamp V_{out1})

* Is $V_{out1} = f(R_{AC})$?

Do we have feedback?

NFB (clue: Dink the output & figure out)

Golden rule #2 applies: $U^- = U^+$

Voltage across $R_{AC} = U^- = U^+ = 0$, No current through R_{AC}

$V_{out1} \neq f(R_{AC})$

ii) Find expression for V_{out1} .

Pattern matching? Inverting amplifier


When in doubt → Nodal analysis

Golden rule #1

$$I^+ = I^- = 0$$

$$\text{KCL: } I_R = I_{RAC} + I^- + I_{RAB}$$

$$\Rightarrow I_R = I_{RAB} \quad (I)$$

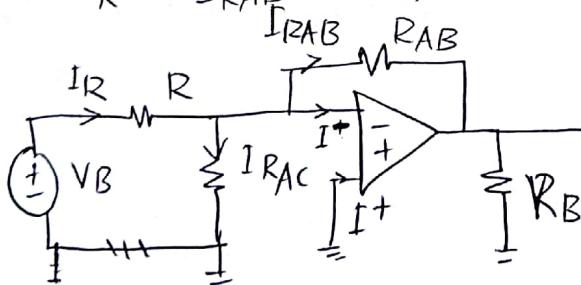

Golden Rule #2

$$U^- = U^+$$

$$\Rightarrow I_{RAC} = \frac{U^- - U^+}{R_{AC}} = 0$$

$$U^+ = 0 \Rightarrow U^- = 0$$

$$I_R = \frac{V_B - U^-}{R} = \frac{V_B}{R} \quad (II)$$

$$I_{RAB} = \frac{U^- - V_{out1}}{R_{AB}}$$

$$\Rightarrow V_{out1} = -I_{RAB}R_{AB} \quad (III)$$

$$(III) \rightarrow V_{out1} = -I_{RAB}R_{AB}$$

$$= -I_R R_{AB} \quad [\text{Using (I)}]$$

$$= -\left(\frac{V_B}{R}\right)R_{AB} \quad [\text{Using (II)}]$$

$$= -\left(\frac{R_{AB}}{R}\right)V_B \quad \rightarrow \text{Inverting amplifier indeed.}$$

iii) Target : $-1.5 \text{ mV} \leq V_{\text{out1}} \leq -0.5 \text{ mV}$, have to find R

$$V_B = 5 \text{ V}$$

$$\text{Also : } |I_{RAB}|, |I_{RAC}|, |I_{RBC}| < 100 \mu\text{A}$$

If $V_{\text{out1}} = -\frac{R_{AB}}{R} V_B$, we have.

$$\text{for, } V_{\text{out1}} = -0.5 \text{ mV} \Rightarrow -\frac{R_{AB,\min}}{R} V_B = -0.5 \text{ mV}$$

$$\Rightarrow -\frac{50}{R} \times 5 = -0.5 \text{ mV} \Rightarrow R = 500 \text{ k}\Omega$$

$$\text{For, } V_{\text{out1}} = -1.5 \text{ mV} \Rightarrow -\frac{R_{AB,\max}}{R} V_B = -1.5 \text{ mV}$$

$$\Rightarrow -\frac{150}{R} \times 5 = -1.5 \text{ mV} \Rightarrow R = 500 \text{ k}\Omega$$

Now, are the currents, $< 100 \mu\text{A}$ for worst case scenarios?

$$\rightarrow I_{RAC} = 0 < 100 \mu\text{A} \checkmark$$

$$\rightarrow |I_{RAB,\max}| = \left| \frac{V_{\text{out1},\max}}{R_{AB,\max}} \right| = \frac{V_B}{R} = \frac{5 \text{ V}}{500 \text{ k}\Omega} = 10 \mu\text{A} < 100 \mu\text{A} \checkmark$$

\downarrow
Not a function of R_{AB}

$$\begin{aligned} \rightarrow |I_{RBC,\max}| &= \left| \frac{V_{\text{out1},\max}}{R_{BC,\min}} \right| \\ &= \frac{R_{AB,\max}}{R} V_B \times \frac{1}{R_{BC,\min}} \\ &= \frac{150}{500 \text{ k}} \times 5 \times \frac{1}{50} \\ &= 30 \mu\text{A} < 100 \mu\text{A} \end{aligned}$$

$R = 500 \text{ k}\Omega$
works!

$$b) -1.5mV \leq V_{out1} \leq -0.5mV$$

T_{target}: $500mV \leq V_{out2} \leq 1.5V$, with opamp(1) & resistors(2)

We can see that V_{out2} can be $-1000V_{out1}$

→ Inverting amplifier with a gain of 1000.


Side note:

What if we needed V_{out2} : $-0.5V \leq V_{out2} \leq 0.5V$
and V_{out1} was: $0 \leq V_{out1} \leq 1mV$

$$V_{out2} = 1000V_{out1} - 0.5V$$

Voltage shifter required: See Dis 10A

i)

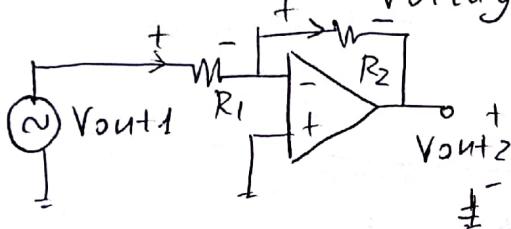

$$R_2 = 1000R_1$$

$$V_{out2} = -\frac{R_2}{R_1}V_{out1}$$

ii) To prevent skin damage

$$\text{Power}(R_1) < 1\mu W \quad [\text{Problem description has } 1\mu W]$$

$$\text{Power}(R_2) < 1\mu W \quad [I \text{ did it with } 10\mu W \text{ in review by mistake! My bad!}]$$

$$\text{Power dissipated in } R_1 = \frac{(V_{diff, R_1})^2}{R_1} = \frac{(V_{out1} - 0)^2}{R_1} = \frac{|V_{out1}|^2}{R_1}$$

$$\text{Power dissipated in } R_2 = \frac{(V_{diff, R_2})^2}{R_2} = \frac{(0 - V_{out2})^2}{R_2} = \frac{|V_{out2}|^2}{R_2}$$

$$\text{Now, } V_{out1} \text{ } P_{R1, \max} < 1\mu W$$

$$\Rightarrow \frac{|V_{out1}|^2 \max}{R_1} < 1\mu W$$

$$\Rightarrow \frac{|-1.5mV|^2}{R_1} < 1\mu W$$

$$\Rightarrow R_1 > 2.25\Omega$$

$$P_{R2, \max} < 1\mu W$$

$$\Rightarrow \frac{|V_{out2}|^2 \max}{R_2} < 1\mu W$$

$$\Rightarrow \frac{1.5^2}{R_2} < 1\mu W$$

$$\Rightarrow R_2 > 2.25M\Omega$$

What if we choose:

$$R_1 = 3k\Omega > 2.25\Omega$$

$$R_2 = 3M\Omega > 2.25M\Omega$$

} Works!


C) $V_w \rightarrow$ voltage signal from wound
 $V_h \rightarrow$ voltage signal from healthy skin
 Target: LED shines brighter ($V_{LED} \uparrow$) when $(V_w - V_h)$ increases.

* Can we use a comparator to compare V_w & V_h ?
 No. Comparators has two levels of voltage.
 We need continuous change in V_{LED}
 We need $V_{LED} = V_w - V_h \rightarrow$ Negative Feedback will work.

How do we approach this problem?

Cookbook shortcut approach:

Inverting amplifier: Example

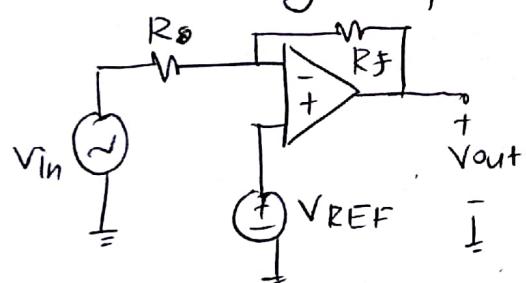


$$V_{out} = V_{in} \underbrace{\left(-\frac{R_f}{R} \right)}_{-ve} + V_{REF} \underbrace{\left(\frac{R_f}{R} + 1 \right)}_{+ve}$$

can make this work.

Choose $R_f = R$,

$$V_{out} = -V_{in} + 2V_{REF}$$

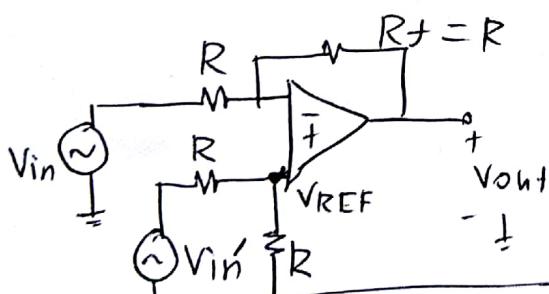Can we make $V_{REF} = \frac{1}{2}V_{in}'$? \rightarrow Voltage divider




For this circuit:

$$V_{out} = V_{in}' - V_{in}$$

Subtraction operation can use this!


Ans:

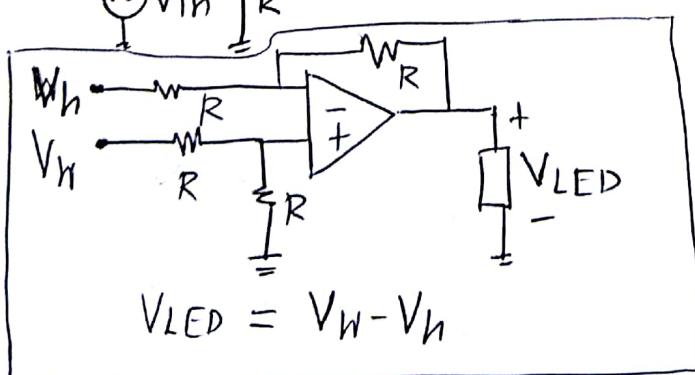

Spring 2018 #6

Some quick terminology I will be using:

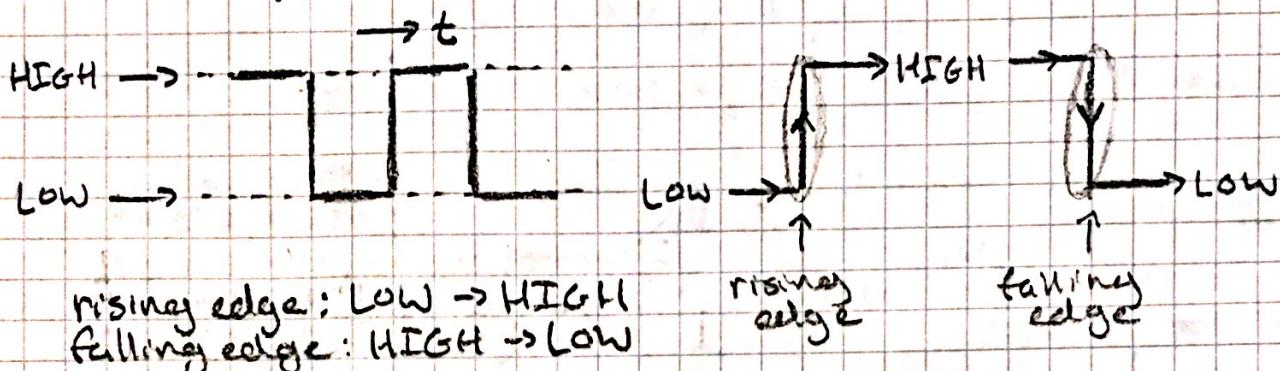for a square wave, which looks like this:




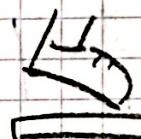a) Want a sensor circuit with specifications:

Jewanna steps off creates a rising edge



output: $V_{out} = 0.5V$
($R_p = 1k\Omega$)




output: $V_{out} = 2V$
($R_p = 10k\Omega$)

We're given a force sensitive resistor such that when Jewanna is on the sensor, $R_p = 1k\Omega$. and when she is off the sensor, $R_p = 10k\Omega$.

We notice that small R_p corresponds to small V_{out} and larger R_p corresponds to bigger V_{out} . What kind of circuit does that sound like?

Voltage divider, where $V_{out} = \frac{R_p}{R + R_p} V_B$

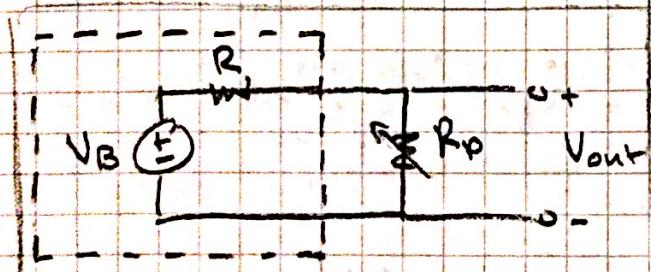We've given this R_p , and a voltage source and other resistors to design the circuit, so let's draw it and solve for R and V_B , our design variables.



rearranging our voltage divider eq.

$$V_{out} R - R_p V_B = -V_{out} R_p$$


$$(0.5)R - (1k)V_B = -0.5k$$

$$(2)R - (10k)V_B = -20k$$


$$\Rightarrow \begin{cases} R = 5k\Omega \\ V_B = 3V \end{cases}$$

We have two sets of R_p, V_{out} , so this is a system of linear equations

b)

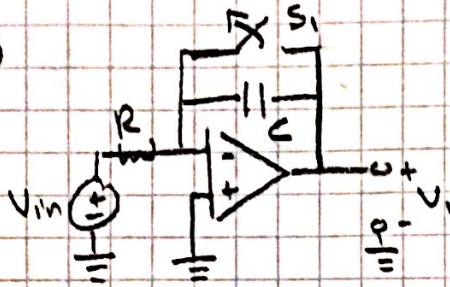


We want V_1 in terms of V_{in} .
 We're given that C is discharged at $t = 0$, and $V_{in} = 0$ at $t = 0$.
 After $t = 0$, V_{in} is a constant.
 Let's look at the cases for S_1 , open and S_1 , closed.

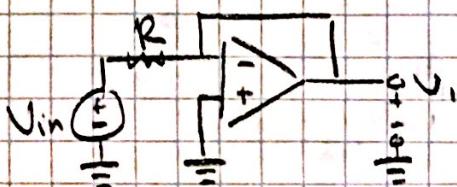 S_1 , closedby golden rules,
we can see

$$V_1 = 0$$

$$t < 0$$

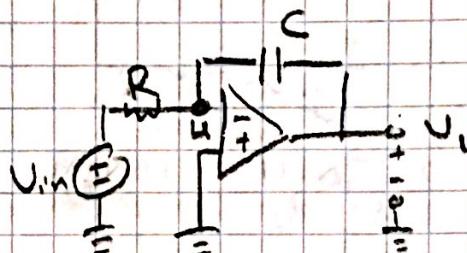 S_1 , open

using nodal analysis at u


$$\frac{V_{in}}{R} = -\frac{C}{dt} \frac{dV_1}{dt}$$

with a negative to account for current direction. Integrating,

$$V_1 = -\frac{1}{RC} \int V_{in} dt = -\frac{1}{RC} (V_{int} + V_{in(0)})$$

$$\Rightarrow V_1 = \frac{1}{RC} V_{int} \quad t \geq 0$$



c)

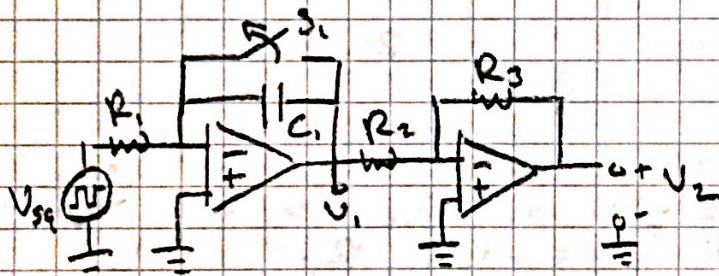


given $R_1 = R_2 = R_3 = 1k\Omega$
 $C_1 = 1\mu F$
 and op-amp noise are
 both $\pm 1V$
 C starts discharged at $t = 0$

since $R_2 = R_3$, the next op-amp circuit is an inverter,
so that $V_2 = -V_1$.


$$\Rightarrow V_2 = \frac{1}{RC} \int V_{sq} dt \quad \text{and } RC = (1k\Omega)(1\mu F) = 1ms$$

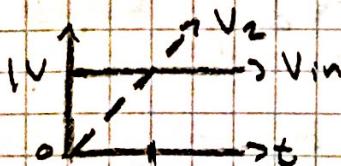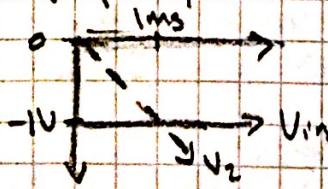for a constant positive input, $RC = 1ms$ for a constant negative input, $RC = 1ms$ 


so then our squarewave input should give us a triangle wave.

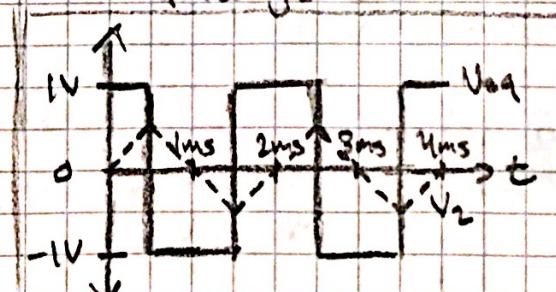note: at $t = \frac{1}{2}ms$, $V_2 = \frac{1}{2}V$
from $V_2 = \frac{1}{RC} V_{int}$.so our peaks are at $\pm \frac{1}{2}V$

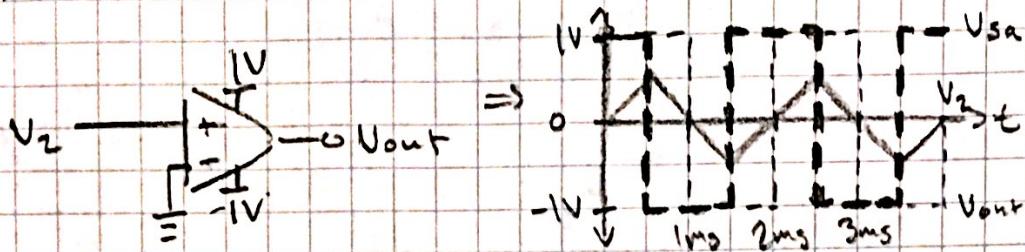d) since we only have resistors and an op amp, our first guess should be a comparator, since the comparator will spit out constant voltages as long as the input voltage doesn't cross V_{ref} in time.




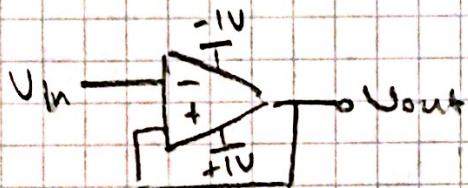almost, but it's shifted in time, so we want a reference voltage that changes depending on the input. We accomplish this with some feedback.




Note: has to be positive feedback because we still want the opamp to rail to give us the squarewave effect. Only constant voltages.

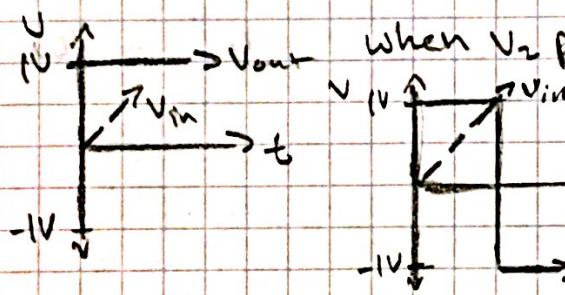so assume U_{out} starts higher than V_{in} .



then U_{out} rails to the bottom because of the comparator effect, since now $V^- > V^+$. We can see how to get the edges at the peaks of a triangle wave.

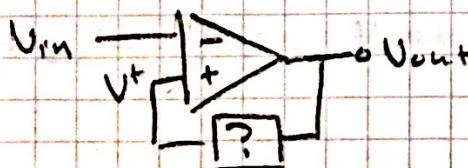
but our V_2 only reaches up to $\frac{1}{2}V$ and $-\frac{1}{2}V$, so we need to lower the feedback input (V^+), since we can't raise the V_2 peak (we only have one op-amp)



so how do we scale down U_{out} so that V^+ will switch at the V_{in} peaks?

Voltage Divider! we know max/min are $\pm 1V$, and the input peaks are $\pm \frac{1}{2}V$,

so we want $V^+ = \frac{1}{2}U_{out}$

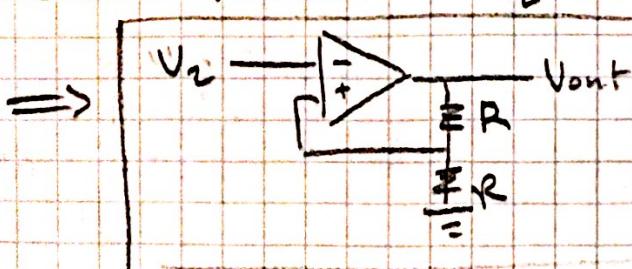

e) pulses have a period of 2ms, so when Jewanna starts running, the pulses start going, and when she finishes, the switch switches back and the V_2 goes back to zero, stopping the pulses.

total time is then # pulses \times pulse period