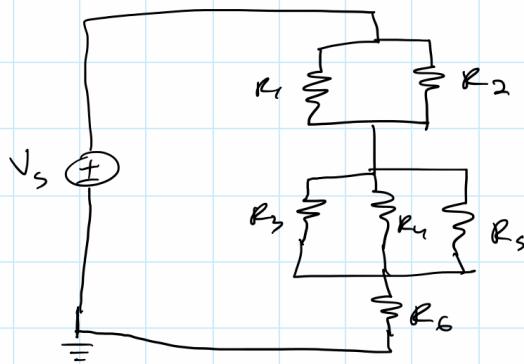


Fast Nodal Analysis Guide


Wednesday, October 24, 2018 7:14 PM



Question: Find the potentials/voltages/currents at every point.

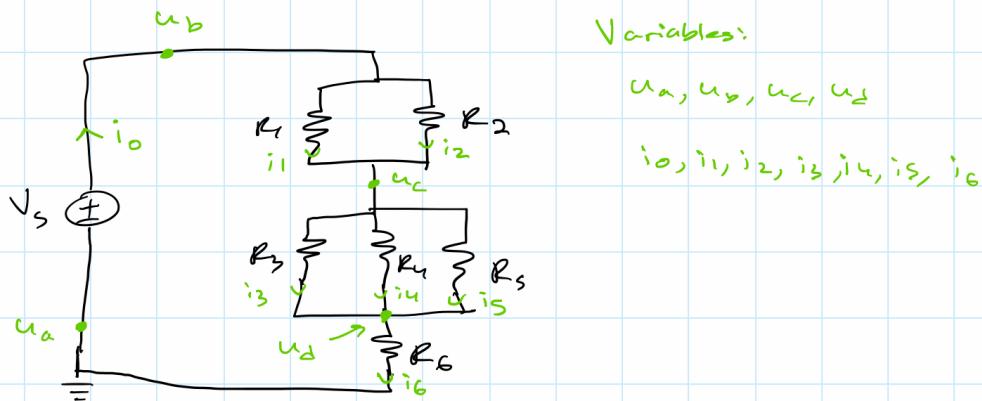Problem: Using our standard method of labelling

Currents & potentials, we run into a whole lot of variables!



Variables:

u_a, u_b, u_c, u_d

$i_{10}, i_{11}, i_{12}, i_{13}, i_{14}, i_{15}, i_{16}$

Idea: Do we really need to solve for all the variables or can we simplify what we are solving for?


Hint: We only need to solve for one type of variable

(i.e. solve for only potentials or currents).

Which one is "better" to solve??

(Try to answer before class - relation between?)

<

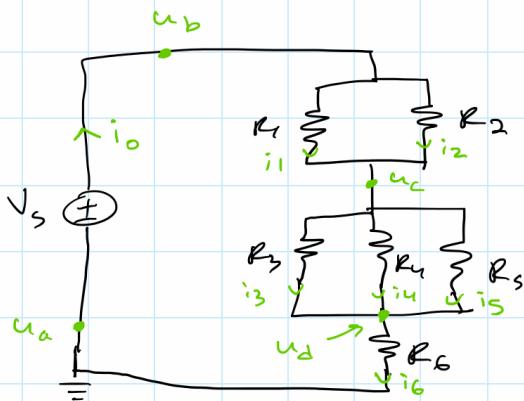

Variables:

 u_a, u_b, u_c, u_d $i_0, i_1, i_2, i_3, i_4, i_5, i_6$


Idea: Do we really need to solve for all the variables or can we simplify what we are solving for?
 Hint: We only need to solve for one type of variable (i.e. solve for only potentials or currents).
 Which one is "better" to solve??
 (Try to answer before seeing solution below)

Solution: Solving for potentials is better! That way

if we ever want to solve for some current

through a resistor, we can use $V = IR$, and directly substitute u 's to get $i_R = \frac{u_t - u_-}{R}$.

Ex:

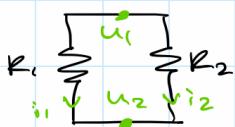

If we have solved for the potentials, we know the u 's.

$$V = IR \Rightarrow I = \frac{V}{R}$$


$$\therefore i_1 = \frac{u_t - u_2}{R_1}, \quad i_2 = \frac{u_t - u_2}{R_2}$$

Note $\frac{u_t - u_2}{R_1}$ & NOT $\frac{u_2 - u_t}{R_1}$ due to passive sign convention

Okay, back to the original problem.



Okay, back to the original problem.

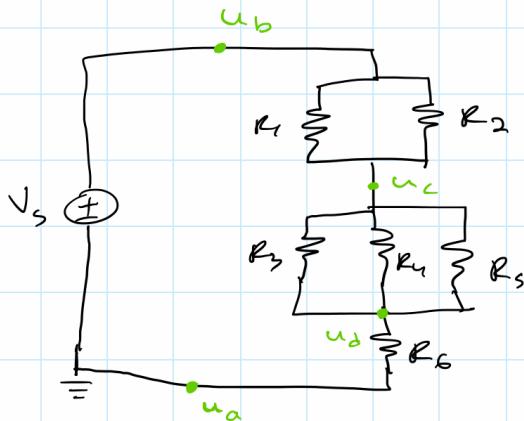

We want to only have potential variables.

Voltages:

u_a, u_b, u_c, u_d

Note how u_a is on the wire connected with ground, so

$$u_a = 0.$$

Can we solve for anything else?

Note that u_a and u_b are separated by a voltage source, so $u_b = u_a + V_s$ (or $u_b - u_a = V_s$).

We now have $u_a = 0$, $u_b = V_s$, how can we solve


for u_2 & u_3 ? ★ This is really nice! Before we had to solve for 4 variables, now we only have 2!! ★

Solution: Use KCL and substitute $I = \frac{V}{R}$

Imagine this small example:



KCL at node u_b .

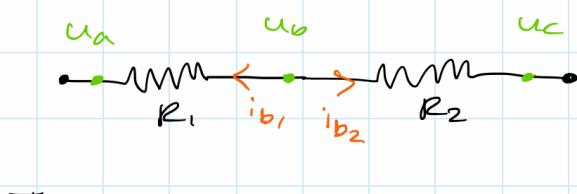




<

Imagine this small example:



KCL at node u_b :

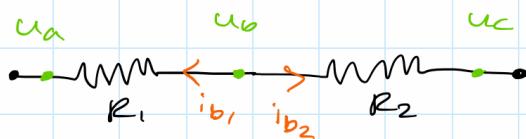

$$I_{out} = I_{in}, \text{ so } i_{b1} + i_{b2} = 0$$

We do not want any current variables, so we can use our buddy Ohm to help us out.


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$i_{b1} = \frac{u_b - u_a}{R_1}, \quad i_{b2} = \frac{u_b - u_c}{R_2}$$


$$i_{b1} + i_{b2} = 0 \Rightarrow \frac{u_b - u_a}{R_1} + \frac{u_b - u_c}{R_2} = 0$$

We got rid of the current variables and only have equations with potentials now!

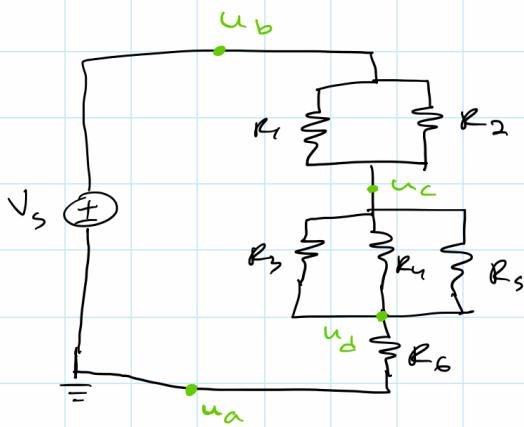
Back one last time to the original question:



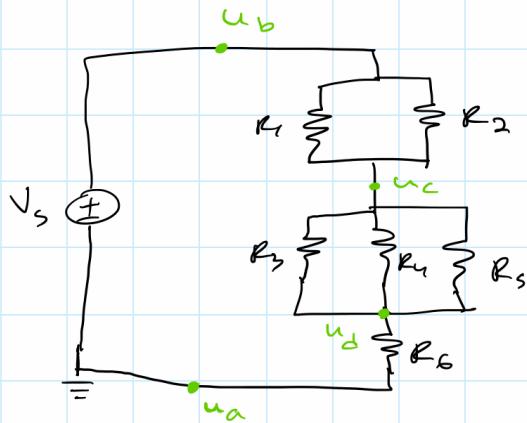Back one last time to the original question:




@ Node u_c :

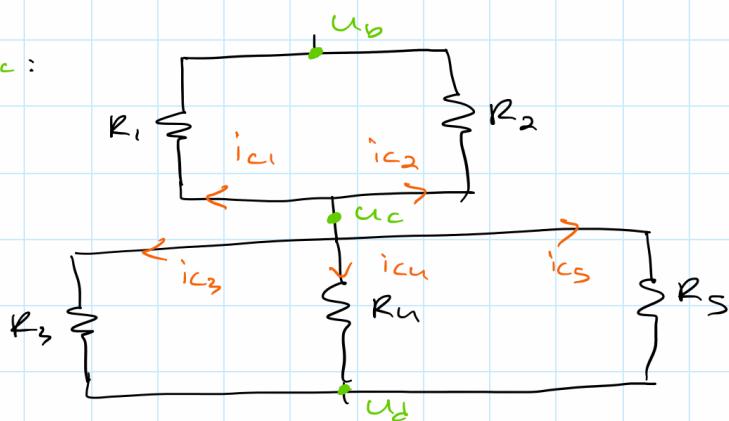

$$i_{c1} + i_{c2} + i_{c3} + i_{cu} + i_{cs} = 0$$

$$\frac{u_c - u_b}{R_1} + \frac{u_c - u_b}{R_2} + \frac{u_c - u_d}{R_3} + \frac{u_c - u_d}{R_4} + \frac{u_c - u_d}{R_5} = 0$$

@ Node u_d :

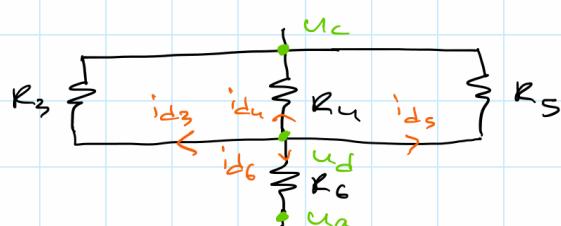


$$i_{d3} + i_{du} + i_{ds} + i_{d6} = 0$$

$$\frac{u_d - u_c}{R_3} + \frac{u_d - u_c}{R_4} + \frac{u_d - u_c}{R_5} + \frac{u_d - u_a}{R_6} = 0$$

In total, we have the following equations:

$$u_a = 0 \quad u_b = u_a + V_s$$

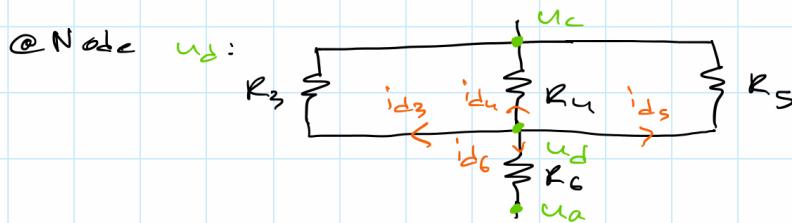

$$id_3 + id_4 + id_5 + id_6 = 0$$

$$\frac{u_d - u_c}{R_3} + \frac{u_d - u_c}{R_4} + \frac{u_d - u_c}{R_5} + \frac{u_d - u_a}{R_6} = 0$$

In total, we have the following equations:

$$u_a = 0, \quad u_b = u_a + V_s$$

$$u_c \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) + u_b \left(-\frac{1}{R_1} - \frac{1}{R_2} \right) + u_d \left(-\frac{1}{R_3} - \frac{1}{R_4} - \frac{1}{R_5} \right) = 0$$

$$u_d \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} \right) + u_c \left(-\frac{1}{R_3} - \frac{1}{R_4} - \frac{1}{R_5} \right) + u_a \left(-\frac{1}{R_6} \right) = 0$$

4 unknowns & 4 variables so we can solve!

Note that 2 of the variables are "trivial" ($u_a = 0, u_b = V_s$),

so we have more like 2 unknowns & 2 equations!

We can then solve using our matrix methods or by

direct substitution/elimination (the latter is usually easier).

Good, so what were the steps we did?

① Label nodes

② Get relations for all nodes connected to voltage sources

③ "Modified KCL" on all nodes not in step 2


④ Solve

We will now go through some examples. I encourage you to try to set up the equations for each circuit before going through the solutions.



<

Example 1:

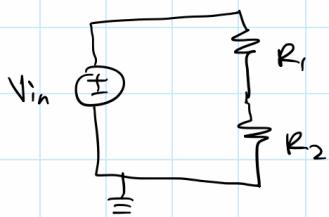

Step 1: Label nodes


Step 2: Get relations for all nodes

connected to voltage sources

Step 3: "Modified" KCL on all nodes
not in step 2.

Step 4: Solve!

Step 1:

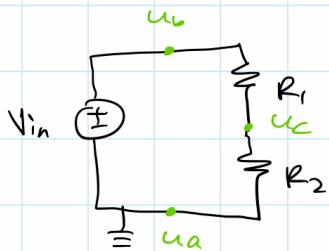

Step 2:

$$u_a = 0, \quad u_b - u_a = V_{in}$$

Step 3:

$$\frac{u_c - u_b}{R_1} + \frac{u_c - u_a}{R_2} = 0$$

Note we are skipping writing
 $i_{c1} + i_{c2} = 0$ but that is
 implicitly what we are doing.

Step 4: $u_a = 0$

$$u_b - u_a = V_{in} \Rightarrow u_b = u_a + V_{in} = 0 + V_{in} = V_{in}$$

$$\frac{u_c - u_b}{R_1} + \frac{u_c - u_a}{R_2} = 0 \Rightarrow \frac{u_c - V_{in}}{R_1} + \frac{u_c - 0}{R_2} = 0$$


$$\Rightarrow u_c \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{in}}{R_1}$$

$$\Rightarrow u_c \cdot \left(\frac{R_1 + R_2}{R_1 \cdot R_2} \right) = \frac{V_{in}}{R_1} \Rightarrow u_c = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$


We got our regular voltage divider equation!

Example 2:

Find the potential at each node.

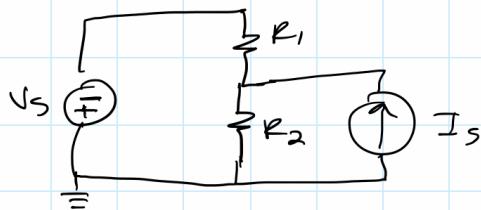

Solution:

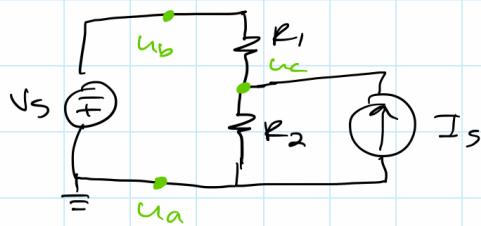

Note the negative as $(-)$ instead of

\swarrow usual (\mp) !!!

$$u_a = 0$$

$$\underline{u_a - u_b = V_s} \Rightarrow 0 - u_b = V_s \Rightarrow u_b = -V_s$$

positive side of voltage source — negative side = voltage source

$$@ \text{Node } u_c: \frac{u_c - u_b}{R_1} + \frac{u_c - u_a}{R_2} = I_s \quad (\text{I}_{\text{out}} = \text{I}_{\text{in}})$$

\Leftarrow Don't be scared by the

current source, just think about how it affects the KCL equation!

Solving gets:

$$u_a = 0, \quad u_b = -V_s$$

$$u_c \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = I_s + \frac{u_b}{R_1} + \frac{u_a}{R_2} \Rightarrow$$

$$u_c \left(\frac{R_1 + R_2}{R_1 R_2} \right) = I_s - \frac{V_s}{R_1} \Rightarrow$$

$$u_c = \left(I_s - \frac{V_s}{R_1} \right) \cdot \frac{R_1 R_2}{R_1 + R_2}$$


If we then wanted to solve for the current through R_1 , we

can use Ohm's law and get $i_1 = \frac{u_a - u_c}{R_1}$ (or $\frac{u_c - u_a}{R_1}$ depending on

direction of i_1) and substitute for u_a & u_c from above equations.

Example 3:


Solve for potentials at each node.

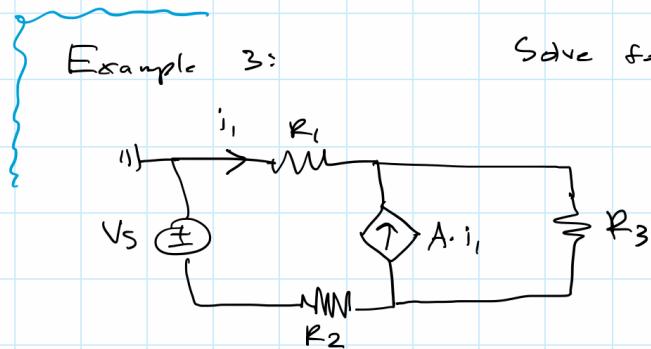

$$V_s = 5$$

$$R_1 = 1, R_2 = 2, R_3 = 3, A = 4$$

Solution:

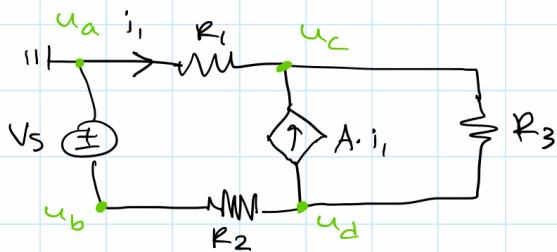

$$\begin{aligned} u_a &= 0, \quad u_a - u_b = V_s, \quad i_1 = \frac{u_a - u_c}{R_1} \\ \frac{u_c - u_a}{R_1} + \frac{u_c - u_d}{R_3} &= A \cdot i_1, \quad \frac{u_d - u_b}{R_2} + A \cdot i_1 + \frac{u_d - u_c}{R_3} = 0 \end{aligned}$$

We have 5 equations and 5 unknowns (i_1 counts as an unknown), so we can subsequently solve to get a unique solution.

$$\textcircled{1} \quad [u_a = 0]$$

$$\textcircled{2} \quad u_a - u_b = 5 \Rightarrow 0 - u_b = 5 \Rightarrow [u_b = -5]$$

$$\textcircled{3} \quad i_1 = \frac{0 - u_c}{1} = -u_c$$


$$\textcircled{4} \quad \frac{u_c - 0}{1} + \frac{u_c - u_d}{3} = 4 \cdot (-u_c) \Rightarrow u_c + \frac{1}{3}u_c - \frac{1}{3}u_d = -4u_c \Rightarrow \frac{16}{3}u_c = \frac{1}{3}u_d \\ \Rightarrow u_c = \frac{1}{16}u_d \text{ or } 16u_c = u_d$$

$$\textcircled{5} \quad \frac{u_d - (-5)}{2} + 4 \cdot (-u_c) + \frac{u_d - u_c}{3} = 0 \Rightarrow \frac{u_d}{2} + \frac{5}{2} - 4u_c + \frac{u_d}{3} - \frac{u_c}{3} = 0 \\ \Rightarrow -\frac{13}{3}u_c + \frac{5}{2} + \frac{5}{6}u_d = 0$$

$$\text{Substituting } u_d = 16u_c \Rightarrow -\frac{13}{3}u_c + \frac{5}{2} + \frac{5}{6} \cdot 16u_c = 0$$

$$\Rightarrow -\frac{13}{3}u_c + \frac{5 \cdot 8}{3}u_c = -\frac{5}{2} \Rightarrow \frac{27}{3}u_c = -\frac{5}{2} \Rightarrow [u_c = -\frac{5}{18}]$$
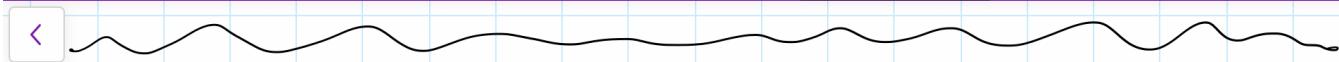
$$u_d = 16u_c = 16(-\frac{5}{18}) \Rightarrow [u_d = -\frac{40}{9}], \quad i_1 = -u_c \Rightarrow [i_1 = \frac{5}{18}]$$



Main takeaways

- Try to only solve for potentials
- 4 steps:
 - Label nodes
 - Relations with voltage sources

★ Modified KCL ★

(Food for thought, how can we handle
circuits with capacitors using this technique?)

- Solve!
- Try to get a systematic approach in attacking circuit analysis problems!